



1

Cross Correlation

Question

Solution

Video

Discussion

Alice wants to design a circuit which takes two serial inputs `sig_x_i` and `sig_y_i` such that the input `s`: circuit produces an output `z_o` which is asserted whenever there is an expectation of seeing a 1 on the `s`

All the flops should be positive edge triggered with asynchronous reset (if any).

Interface Specifications

- The interface guarantees that a 1 on `sig_x_i` will be seen on input `sig_y_i` within 32-clock cycle

Interface Definition

`sig_x_i`: Serial **input** to the **module**

`sig_y_i`: Serial **input** to the **module**

`z_o` : Single **bit output** which is ``1`` whenever there is an expectation of seeing a ``1`` on the **input** `sig_y_i`

Sample Waveform

